

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FOURTH SEMESTER B.TECH DEGREE EXAMINATION 2016

Course Code: IC 202

Course Name: Linear Systems and networks

Model Question Paper

Max.marks:100

Duration: 3 Hours


PART-A

(Answer Any Two)

1. (a) What are the advantages and disadvantages of open and closed loop control system?

(5Marks)

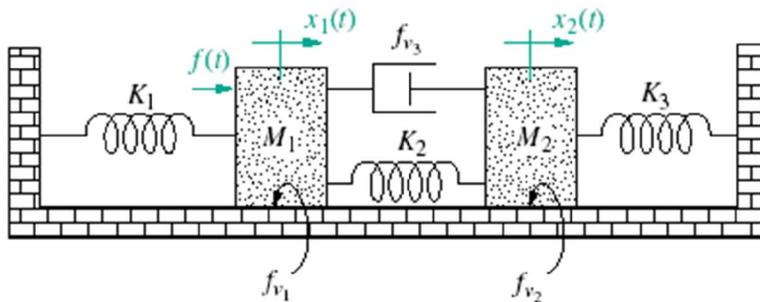(b) Obtain the transfer function $X_2(S)/F(S)$ for the system shown below



(10Marks)

2.(a) Derive the differential equation and obtain the transfer function $E(S)/\theta(S)$ for an armature controlled DC motor coupled to a mechanical load having inertia 'J' and a viscous friction coefficient 'b'. (10Marks)

$$G(s) = \frac{(s^2 + 9)(2 + 5s)}{(s^2 + 16)(2 + 3s)}$$

(b) Find the poles and zeros of the function

(5Marks)

3.(a) What is meant by poles and zeros of a system's transfer function? Explain


(4Marks)

(b) Explain the relation between impulse response and transfer function of a system.

(3.5Marks)

(c) Consider the liquid level system shown below. Obtain its transfer function $H(S)/Q(S)$

(7.5Marks)

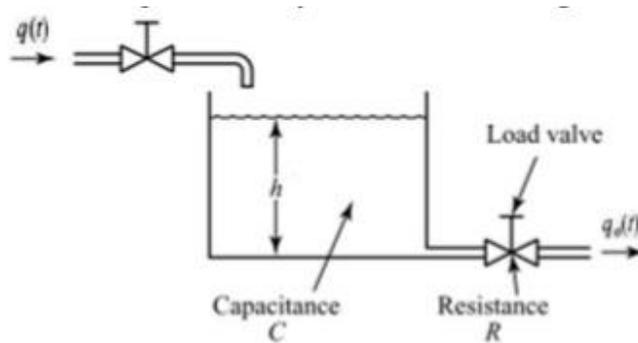

Part – B

(Answer Any Two)

4. Derive the DC response of RL,RC,RLC.
5. Explain the following
 - a. Initial conditions of R,L, C
 - b. Final condition of R,L, C
 - c. Time constant from the DC response of RL circuit.
6. Derive the following
 - a. Sinusoidal response of RC and RLC circuit
 - b. Time constant from the DC response of RC circuit (2x15)


Part – C

(Answer Any Two)

7. Answer the following
 - a. Restrictions of poles and zeros locations for driving point function and transfer functions.
 - b. Derive time domain behavior from pole zero plot of given transfer function.

$$I(s) = \frac{(s+2)}{(s+1)(s+5)}$$

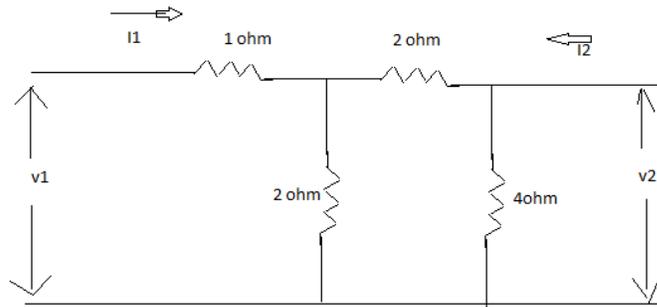8. Answer the following
 - a. Derive Short circuit and open circuit parameters
 - b. Obtain the hybrid parameter for the following circuit.



9. Obtain a) the relationship between Z and Y parameters.

b) Find the response from pole zero plot and verify for the following Voltage.

$$V(s) = \frac{(s+5)}{(s+1)(s+6)} \quad (2 \times 20)$$